

CSCI 3130

Homework 6

Due: Feb. 28, 10:00 PM

1. (2 points) What are the fundamental differences between combinational circuits and sequential circuits?

Combinational Circ


input \Rightarrow output
ie: feed forward

Seq. Circ


input + current output \Rightarrow ^{next} output
ie: feed back

2. (3 points) Draw the **blackbox** diagrams for the three flip-flops studied in class (SR, D, and JK).


SR flip flop

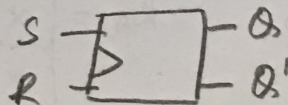

D flip flop

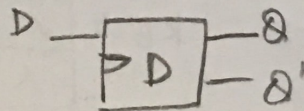

JK flip flop

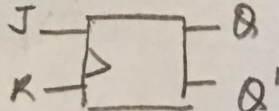

3. (2 points) Positive-edge D and JK flip-flops only update their internal state when the clock goes from 0 (low-voltage) to 1 (high-voltage) True or False?

True

4. (8 points) **Sequential Circuit** - Design a unsigned 2-bit counter using J-K flip-flops that increments by one on each clock cycle 0,1,2,3,0,1,2,3,0,... unless an external input R is turned on, which will reset the counter to 0 instead. You need to show the truth table for the circuit and find a simplified expression for each output using a K-map. Show ALL of your work and draw the final circuit.

C	A	B	A	B	JA	KA	JB	KB
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	X	0
0	1	0	1	0	X	0	0	X
0	1	1	1	1	X	0	X	0
1	0	0	0	1	0	X	1	X
1	0	1	1	0	1	X	X	1
1	1	0	1	1	X	0	1	X
1	1	1	0	0	X	1	X	1

$$J_A = \begin{array}{|c|c|c|c|} \hline 0 & 0 & X & X \\ \hline 0 & 1 & X & X \\ \hline \end{array} = CB$$

$$K_A = \begin{array}{|c|c|c|c|} \hline X & X & 0 & 0 \\ \hline X & X & 1 & 0 \\ \hline \end{array} = J_A$$

$$J_B = \begin{array}{|c|c|c|c|} \hline 0 & X & X & 0 \\ \hline 1 & X & X & 1 \\ \hline \end{array} = C$$

$$K_B = \begin{array}{|c|c|c|c|} \hline X & 0 & 0 & X \\ \hline X & 1 & 1 & X \\ \hline \end{array} = J_B$$

